

MADVLSI: MP1 Report

Lauren Xiong

September 12, 2023

In Mini Project 1, I made a schematic diagram of an AND gate in xschem, a transistor layout design of the AND gate in Magic, and used Netgen to compare the differences between the two designs.

1 Schematic Capture and Simulation

Figure 1 shows the highest level of schematic diagram of the AND gate in xschem. It consists of two subcircuits, which are the NAND gate shown in Figure 2 and the inverter shown in Figure 3.

Figure 4 shows the schematic diagram of the AND gate that contains transient simulation configurations. The results of the simulation is shown in Figure 5.

2 Layout Design

The layout of the AND gate in Magic is shown in Figure 6.

3 Layout Versus Schematic

The layout versus schematic (LVS) output showed that the two circuits made in xschem and Magic matched up. The file can be accessed [here](#).

4 Design files

All the design files of MP1 can be accessed [here](#).

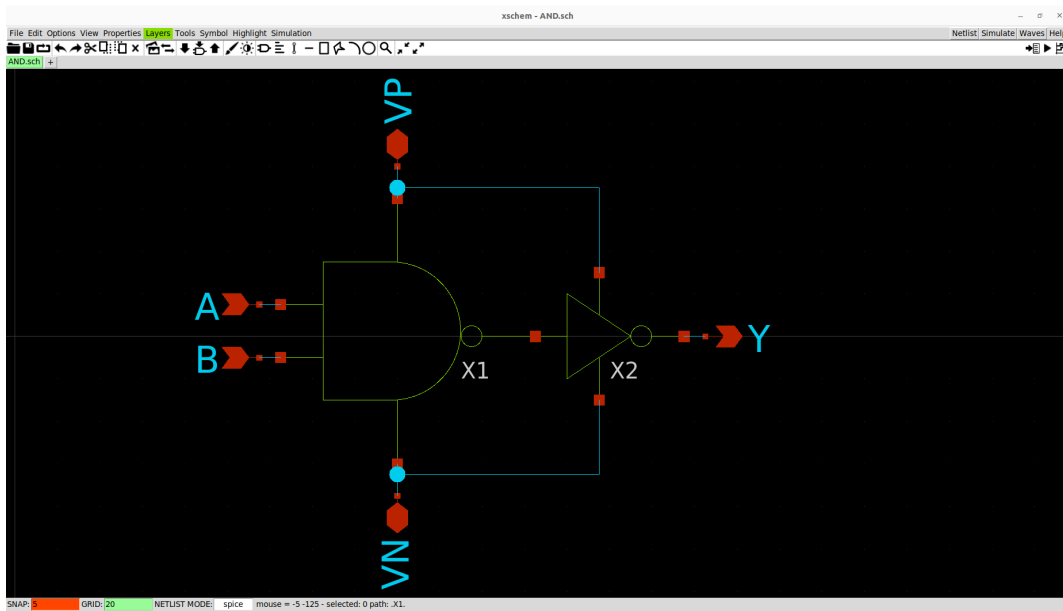


Figure 1: AND gate high level schematic diagram.

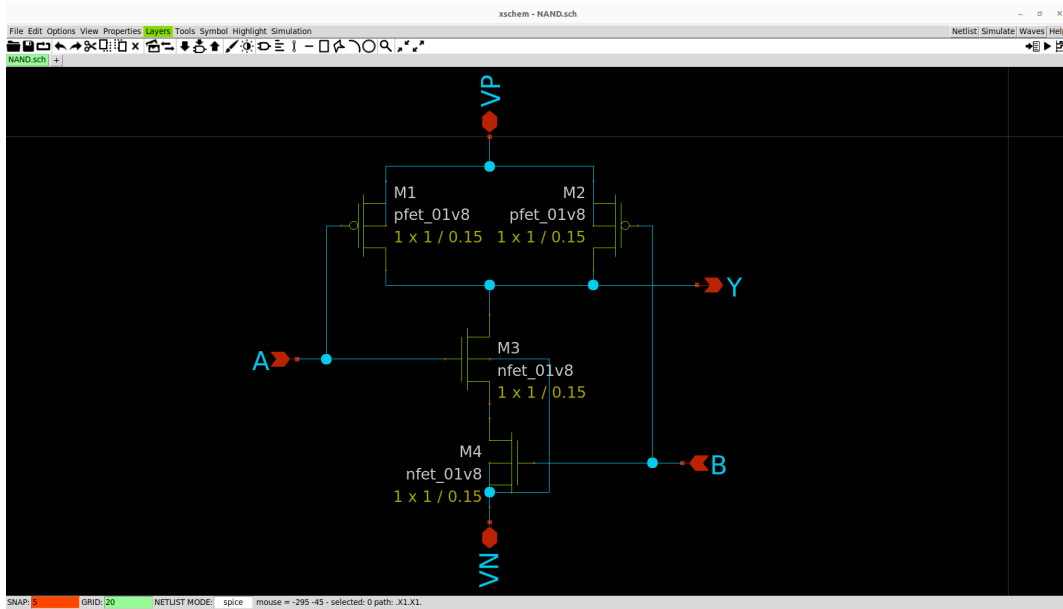


Figure 2: NAND gate schematic diagram.

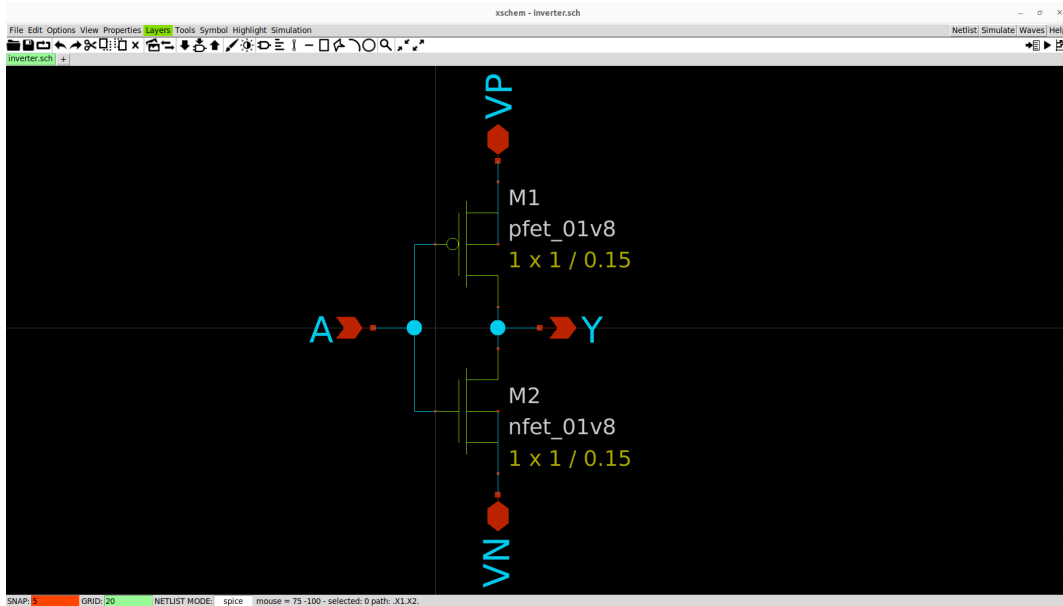


Figure 3: Inverter schematic diagram.

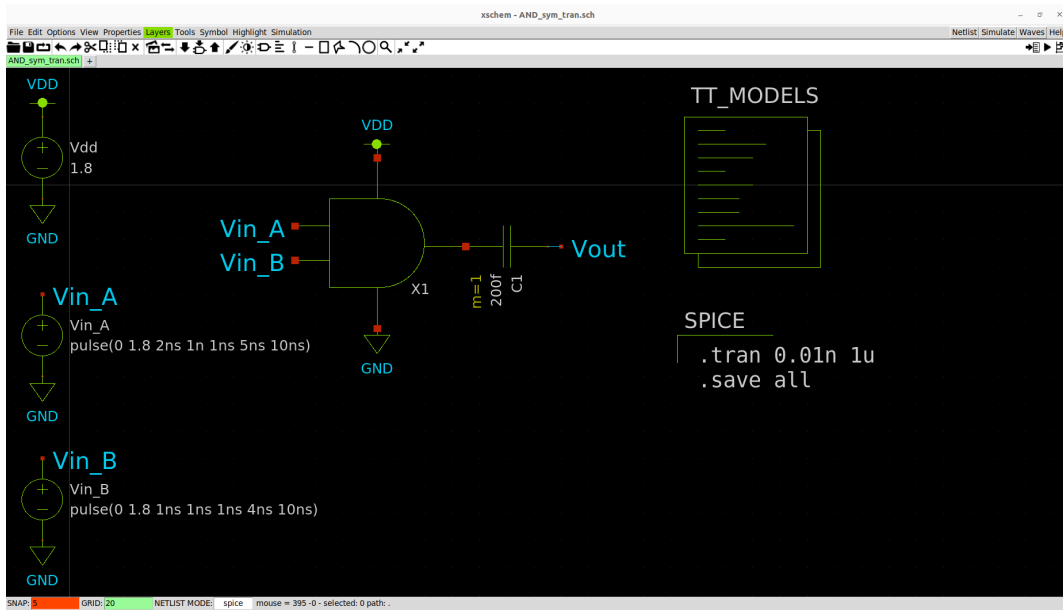


Figure 4: Simulation schematic diagram of the AND gate.

 


Figure 5: Transient simulation results.

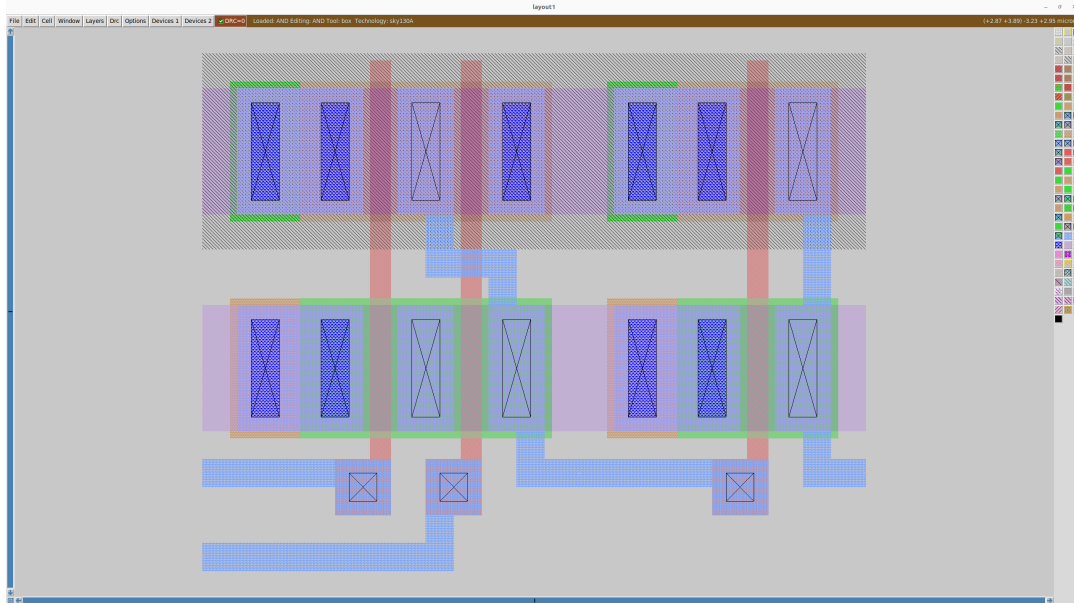


Figure 6: Layout of AND gate in Magic.